
Data stored as 1D array.

Internal Mem


RAM , ROM

S / \ D

IC

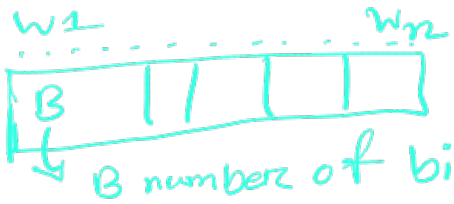

mem size = W words × B bits.

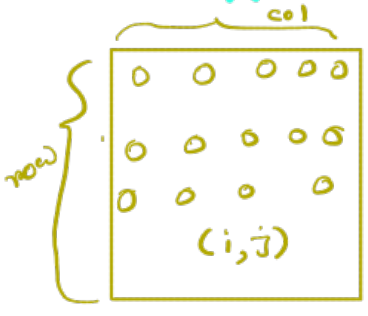


2 diff Address by address bus.

16 Mbit

4 bit → 1 word

↓ L→ data bus with.

distributed in 4 diff. chip.

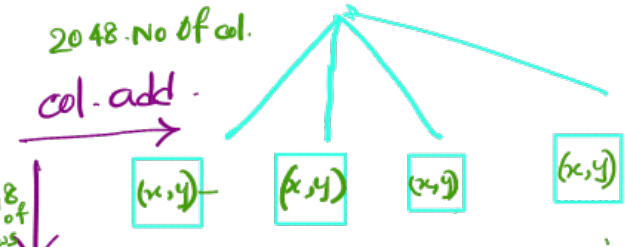

same xy in all chips as 4 bit distributed in all

11 bit add.

2d format

Size $\frac{4\text{Mbit}}{2} = 2\text{Mbit}$

↳ lrow = lcol.

lrow = must lcol

↓ length.

2048×2048

$= 2^{11} \times 2^{11}$

$=$

$= 2^{2} \times 2^{20}$

$= 4M$.

°increase 1 bit, capacitance will increase by what?

$$\frac{11\text{bit} + 1}{2048}$$

optimize →

destructive read →